
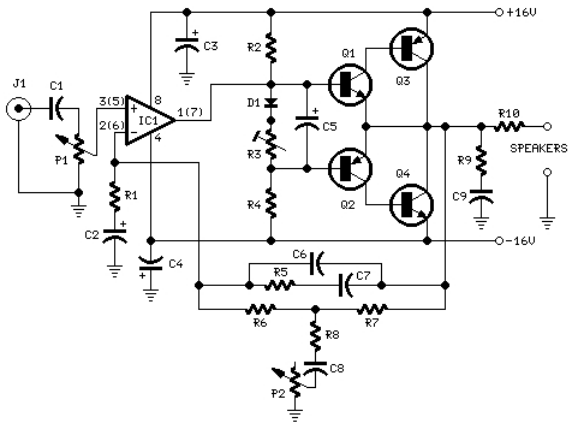


CIRCUITS, CATEGORIES AND REWRITE RULES

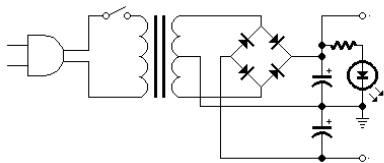

John Baez & Brendan Fong
Higher-Dimensional Rewriting and Applications
Warsaw, 29 June 2015

If mathematicians want to understand networks, a good place to start is electrical circuits.




They look like string diagrams for morphisms in symmetric monoidal categories... *and they are!* Their mathematics is well-studied, but not yet fully formalized. The modern world is *made of them*.

To keep things simple, today let's just talk about circuits made of resistors — a special case of my work with [Brendan Fong](#).


We will:

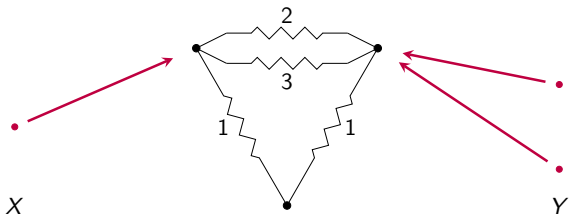- ▶ Describe a category **Circ** where morphisms are electrical circuits made out of resistors.



- ▶ Describe the 'black box functor' $\blacksquare: \mathbf{Circ} \rightarrow \mathbf{FinRel}_{\mathbb{R}}$ sending each circuit to its 'behavior': the linear relation it imposes between electric potentials and currents at its inputs and outputs.
- ▶ Study rewrite rules that go between circuits with the same behavior.

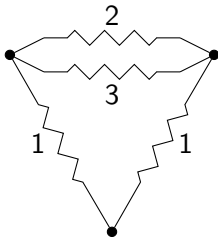For today, define a **circuit** to be a graph with edges labelled by positive real numbers called **resistances**:



More precisely, we have:

- ▶ a directed graph $s, t: E \rightarrow N$ with a set of **edges** E and a set of **nodes** N , each edge $e \in E$ having a **source** $s(e) \in N$ and **target** $t(e) \in N$,
- ▶ a **resistance** for each edge: $r: E \rightarrow (0, \infty)$.

When we use it, a circuit has:

- ▶ a **potential** $\phi(n) \in \mathbb{R}$ at each node $n \in N$:

$$\phi: N \rightarrow \mathbb{R}$$

- ▶ a **current** $I(e) \in \mathbb{R}$ along each edge $e \in E$:

$$I: E \rightarrow \mathbb{R}$$

These obey some linear relations, which is how we get circuits to do interesting things for us.

If we fix the potential at some set of **terminals** $T \subseteq N$, the circuit automatically chooses potentials at all the other nodes, and currents along all the edges. These obey:

- ▶ **Ohm's law**: the current along an edge is proportional to the change in potential as we go from its source to its target:

$$I(e) = \frac{\phi(s(e)) - \phi(t(e))}{r(e)}$$

- ▶ **Kirchhoff's current law**: the total current flowing out of a node $n \in N - T$ equals the total current flowing in:

$$\sum_{e \text{ such that } s(e)=n} I(e) = \sum_{e \text{ such that } t(e)=n} I(e)$$

At the terminals there can be a net inflow or outflow of current!

That is, if we define the **current flowing out of the node** n by:

$$I(n) = \sum_{e \text{ such that } s(e)=n} I(e) - \sum_{e \text{ such that } t(e)=n} I(e)$$


then $I(n) = 0$ if $n \in N - T$, but $I(n)$ can be nonzero if $n \in T$.

For example, this simple circuit with two terminals can have current flowing into $s(e)$ and out of $t(e)$:



$$I(e) = \frac{\phi(s(e)) - \phi(t(e))}{r(e)}$$

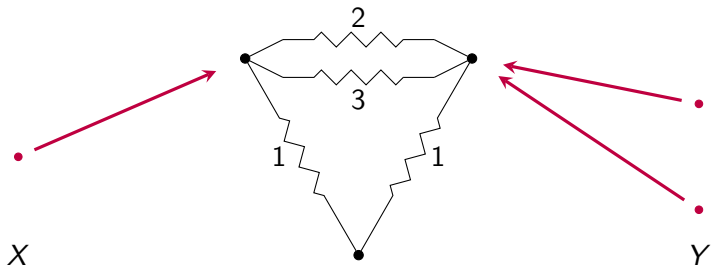Define an **open circuit** to be a circuit with chosen **inputs** and **outputs**:



picked out by maps

$$i: X \rightarrow N$$

$$o: Y \rightarrow N$$

Here the terminals are $i(X) \cup o(Y)$.

Thanks to Ohm's law and Kirchhoff's current law, an open circuit imposes linear equations relating:

- ▶ the potentials at the inputs and currents flowing *into* the inputs:

$$\phi(i(x)), -I(i(x)) \quad \text{for } x \in X$$

and:

- ▶ the potentials at the inputs and currents flowing *out of* the outputs:

$$\phi(o(y)), I(o(y)) \quad \text{for } y \in Y$$

Thus, it picks out a linear subspace

$$L \subseteq (\mathbb{R}^X \oplus \mathbb{R}^X) \oplus (\mathbb{R}^Y \oplus \mathbb{R}^Y)$$

describing the allowed potentials and currents at inputs and outputs.

The linear subspace

$$L \subseteq (\mathbb{R}^X \oplus \mathbb{R}^X) \oplus (\mathbb{R}^Y \oplus \mathbb{R}^Y)$$

defined by an open circuit with inputs X and outputs Y is a morphism

$$L: \mathbb{R}^X \oplus \mathbb{R}^X \rightsquigarrow \mathbb{R}^Y \oplus \mathbb{R}^Y$$


in the category $\mathbf{FinRel}_{\mathbb{R}}$ of finite-dimensional real vector spaces and linear relations. We call this the circuit's **behavior**. It says what the circuit does 'as seen from outside'.

This suggests finding a category **Circ** whose morphisms are open circuits, and a functor


$$\blacksquare: \mathbf{Circ} \rightarrow \mathbf{FinRel}_{\mathbb{R}}$$

mapping each open circuit to its behavior.

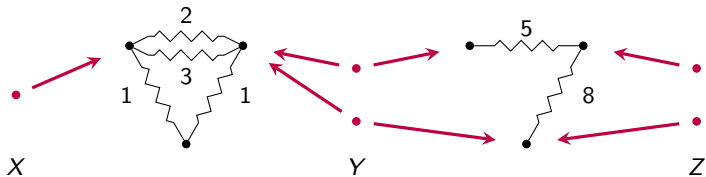We can compose open circuits by gluing the outputs of one to the inputs of another. These open circuits:




compose to give this:

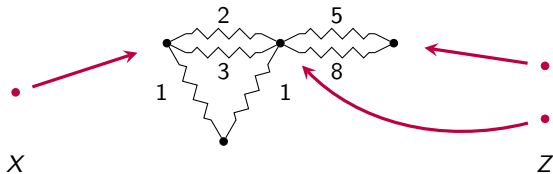


Indeed, there is a category **Circ** where:

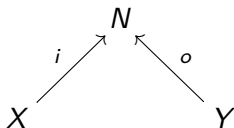- ▶ objects are finite sets
- ▶ a morphism $f: X \rightarrow Y$ is an isomorphism class of open circuits from X to Y . An **open circuit from X to Y** is a cospan of finite sets




where N is the nodes of a graph $s, t: E \rightarrow N$ with edges labelled by resistances via $r: E \rightarrow (0, \infty)$.

We can also 'tensor' open circuits:

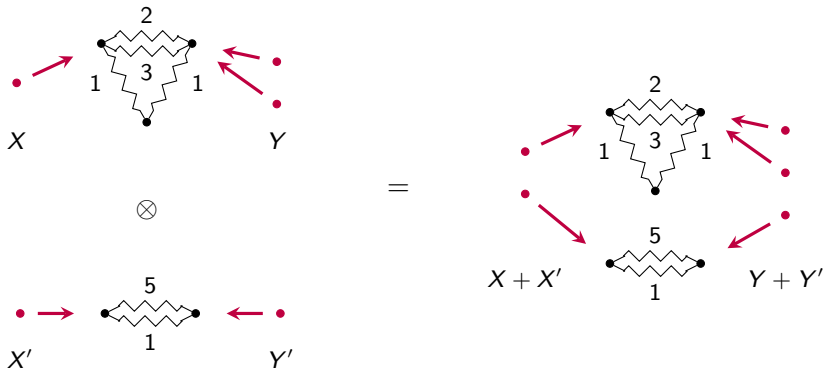


How do we prove **Circ** is a symmetric monoidal category? We can use [Fong's theory of decorated cospans](#).

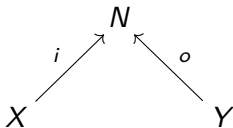Say we start with a category **C** with finite colimits: in our example, **C** = **FinSet**. We can make a bicategory where morphisms are cospans in **C**:




and composition is done by pushout:

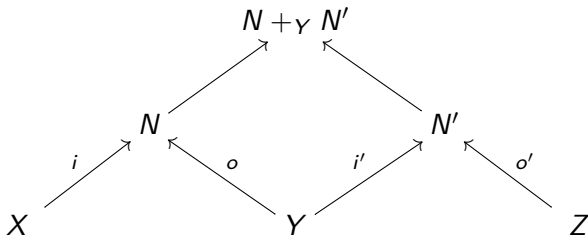

The pushout is defined only up to isomorphism, but there is a category **Cospan**(**C**) where morphisms are *isomorphism classes* of cospans in **C**.

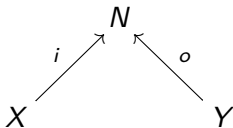If we choose a functor $F: \mathbf{C} \rightarrow \mathbf{D}$, we can try to create a category where a morphism is an isomorphism class of cospans



with N 'decorated' by an element of $F(N)$. In our example, $\mathbf{D} = \mathbf{Set}$ and $F(N)$ is the set of ways of making N into the nodes of a circuit.

But what's an 'element', in general? And how do we 'compose the decorations' when we compose cospans?


Theorem (Fong)

Suppose \mathbf{C} has finite colimits, \mathbf{D} is symmetric monoidal, and

$$F: (\mathbf{C}, +) \longrightarrow (\mathbf{D}, \otimes)$$


is a lax symmetric monoidal functor. Then there is a symmetric monoidal category of **F-decorated cospans**, $\mathbf{FCospan}$, where:

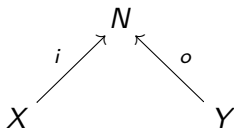- ▶ an object is an object of \mathbf{C} ,
- ▶ a morphism from X to Y is a cospan




together with a **decoration** $r: 1 \rightarrow F(N)$. (Just kidding: actually, a morphism is an isomorphism class of these!)

Given composable morphisms

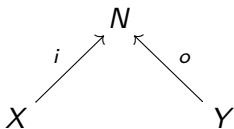

$$r: 1 \rightarrow F(N)$$

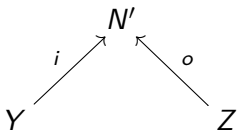

$$r': 1 \rightarrow F(N')$$

we compose the cospans by taking the pushout, and compose the decorations by forming

$$1 \xrightarrow{r \otimes r'} F(N) \otimes F(N') \longrightarrow F(N + N') \longrightarrow F(N +_Y N')$$

where the second arrow comes from F being a *lax* monoidal functor.

So, let $F: (\mathbf{FinSet}, +) \rightarrow (\mathbf{Set}, \times)$ be the lax monoidal functor sending any finite set N to the set of ways of making N into the nodes of a circuit. Then $F\mathbf{Cospan} = \mathbf{Circ}$ is a symmetric monoidal category whose morphisms are open circuits.

This lays the groundwork for the main result:

Theorem (Fong)

There is a symmetric monoidal functor

$$\mathbf{■}: \mathbf{Circ} \rightarrow \mathbf{FinRel}_{\mathbb{R}}$$

mapping any finite set X to the vector space $\mathbb{R}^X \oplus \mathbb{R}^X$, and mapping any open circuit to its behavior.

We can ask various questions about the black box functor, both in our example and for other kinds of circuits:

- ▶ What morphisms are in the image of \blacksquare ? That is: which behaviors can be realized by some circuit?
- ▶ Given a morphism in the image of \blacksquare , how can we find a circuit that gives this morphism? Is there a 'simplest' one?
- ▶ How can we tell if two circuits have the same behavior? Can we find *rewrite rules* that take us between any two circuits with the same behavior? Can we use these to 'simplify' any circuit until we reach a 'normal form'?

The first question is addressed by [our paper](#). The second has been studied in detail for 'planar' circuits.


There is a category **PlanarCirc** where morphisms come from 'planar' open circuits: roughly, open circuits drawn on a square with inputs on top and outputs on bottom. There is again a black box functor

$$\blacksquare: \mathbf{PlanarCirc} \rightarrow \mathbf{FinRel}_{\mathbb{R}}$$

In this case, repeated use of five rewrite rules is enough to carry us from any morphism f to any other morphism g with

$$\blacksquare(f) = \blacksquare(g)$$

1. A **self-loop** can be deleted:

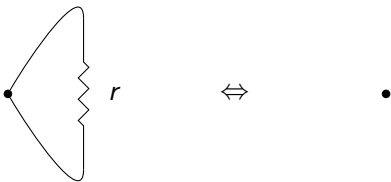

2. A **spike** can be deleted. That is: a unary node that is not a terminal can be deleted along with its incident edge:



unary node that is not a terminal


3. Resistors in **series** can be replaced by a single resistor:



where

$$r = r_1 + r_2$$

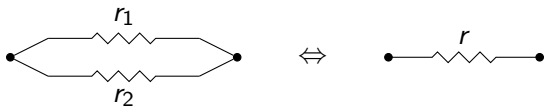
4. Resistors in **parallel** can be replaced by a single resistor:



where

$$\frac{1}{r} = \frac{1}{r_1} + \frac{1}{r_2}$$

5. The **Y- Δ** transform:

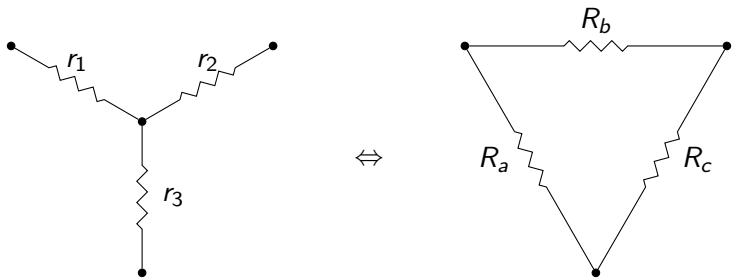

where

$$r_1 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$r_2 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$r_3 = \frac{R_c R_a}{R_a + R_b + R_c}$$

We *cannot* choose directions on these rewrite rules to make them terminating and confluent. So, we don't obtain a 'normal form'.

But there is for each morphism a family of 'best possible forms', and these put a rich mathematical structure on the image of the black box functor!

For details, see:

- ▶ Colin de Verdière, [Réseaux électriques planaires I](#).
- ▶ Colin de Verdière, Gitler and Vertigan, [Réseaux électriques planaires II](#).
- ▶ Curtis, Ingerman and Morrow, [Circular planar graphs and resistor networks](#).
- ▶ Alman, Lian and Tran, [Circular planar electrical networks I: The electrical poset \$EP_n\$](#) .
- ▶ Alman, Lian and Tran, [Circular planar electrical networks II: Positivity phenomena](#).